

AC Circuits and Impedance

In basic DC circuits, along with Kirchoff's laws, the fundamental equation is *DC Ohm's Law*, $V = IR$, relating the voltage and current across a resistor.

In AC circuits, this gets generalized to *AC Ohm's Law*, $V = Iz$. It looks like the DC version, and plays a similar role, but actually more is going on here. In this context V, I, z are all complex numbers.

You'll see why below.

Resistors, Capacitors, Inductors

The three basic (passive, linear) ideal electronic components are the resistor, capacitor, and inductor. At any given time, each can have an instantaneous voltage $V(t)$, and an instantaneous current $I(t)$, across it. The relation between the instantaneous voltages and currents are determined by the electromagnetic physics of the components:

$$\begin{array}{l}
 \begin{array}{c} | \\ \text{R} \\ | \end{array} \quad V(t) = I(t) R \\
 \\
 \begin{array}{c} | \\ \text{C} \\ | \end{array} \quad C \frac{dV(t)}{dt} = I(t) \\
 \\
 \begin{array}{c} | \\ \text{L} \\ | \end{array} \quad V(t) = L \frac{dI(t)}{dt}
 \end{array}$$

For AC circuits, we will assume all voltages are oscillating sinusoidally, and these will turn into equations for the impedance.

Complex Exponentials and Oscillation

Oscillations. An oscillating signal is any signal of the form

$$y(t) = A \cos(\omega t + \delta),$$

which is an arbitrary sinusoidal function. A is called the *amplitude*, and δ is called the *phase shift*.

Due to Euler's identity $e^{i\theta} = \cos \theta + i \sin \theta$, this signal can also be written as


$$y(t) = \text{Re} \left(A e^{i\delta} e^{i\omega t} \right) = \text{Re} \left(Y e^{i\omega t} \right)$$

where we have defined the complex number $Y = A e^{i\delta}$. Y is called the *complex amplitude* of the oscillation $y(t)$, and encodes both the amplitude and the phase by using a single complex number to represent two real numbers. Indeed, $|Y| = A$ and $\phi_Y = \delta$.


To simplify circuit analysis, we can treat all oscillations as complex, taking the real part only at the end. (This is possible when solving any system of linear differential equations with real coefficients.) This lets us forget about the instantaneous quantities $y(t)$, and work with the complex amplitudes Y .

Impedance

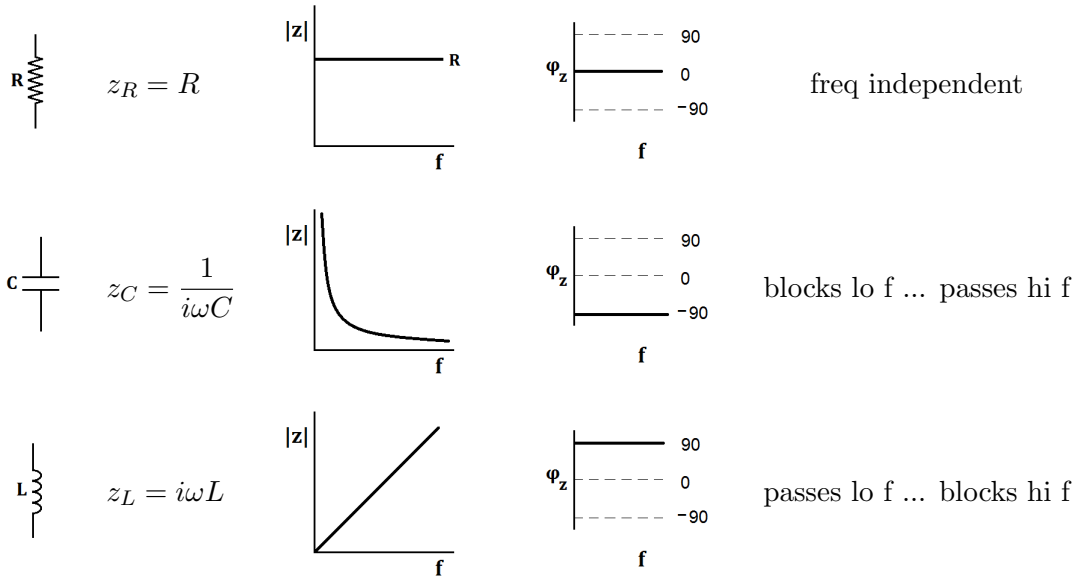We have just deduced the complex impedances for an ideal resistor, capacitor, and inductor:



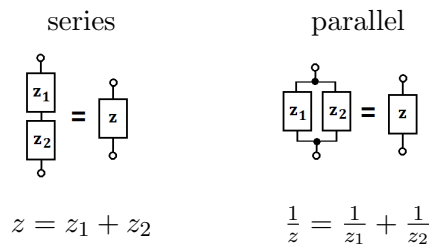It is not hard to show (from Kirchoff's laws) that impedances combine just like DC resistances. In particular:




In this way, more complicated functions $z(f)$ can be built up from the basic impedances.

In general, every passive circuit element will have some impedance $z(f)$, which will vary as a function of frequency. For circuit elements containing a combination of resistance, capacitance, and inductance, $z(f)$ may be a complicated function. This impedance can be measured by measuring the complex amplitudes V and I across a circuit element, since $z = V/I$.

Example. A resistor in series with an inductor has an impedance $z = R + i\omega L$. It follows that the magnitude is $|z| = \sqrt{R^2 + \omega^2 L^2}$ and that the phase is $\phi_z = \tan^{-1}(\frac{\omega L}{R})$. All three quantities are functions of frequency f , where $\omega = 2\pi f$.

Phys 133 Experiment

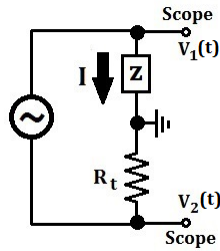

The circuit depicted above can be used to measure the impedance of the circuit element labelled z . R_t is a known resistance (t stands for “test”), and for simplicity let’s denote $R_t = R$ for now.

In its default mode, the oscilloscope screen will display graphs of $V_1(t)$ and $V_2(t)$. For this experiment, change the scope setting to CH2 INVERT ON; now the scope will display $V_1(t)$ and $-V_2(t)$ (note the negative sign, meaning that the graph is flipped upside down). This is not necessary, but it is convenient.

$V_1(t)$ is the voltage across the unknown box, and since $-V_2(t) = I(t)R$, the function $-V_2(t)$ is just a vertically stretched version of the current. Therefore you can visualize the scope’s yellow curve as the voltage across the box, and the blue curve as the current through the box.

From the functions $V(t)$ displayed, we want to extract the complex amplitudes of oscillation. Using the scope’s MEASURE menu, we have the ability to measure the real amplitude of each oscillation, and the relative phase difference between the two oscillations. This is enough to extract the impedance.

Denote the complex amplitudes by V_1 , V_2 , and I . By definition, $z = V_1/I$. But $I = (-V_2)/R$. Therefore

$$z = \frac{V_1 R}{(-V_2)} = \frac{|V_1| R}{|-V_2|} e^{i(\phi_{V_1} - \phi_{(-V_2)})} = \frac{|V_1| R}{|-V_2|} e^{i\delta}$$

where δ is defined as the relative phase difference between $V_1(t)$ and $-V_2(t)$.

We can directly measure $|V_1|$, $|-V_2|$, and δ using the scope, and directly measure R using an ohmmeter, so the formula

$$z = \frac{|V_1| R}{|-V_2|} e^{i\delta}$$

experimentally defines the complex impedance. In particular

$$|z| = \frac{|V_1| R}{|-V_2|} \qquad \phi_z = \delta$$

The preceding method determines z at a fixed frequency. By sweeping through a range of frequencies, one can map out the function $z(f)$.